


31 May

Chapter 2

Boolean Logic

Notes

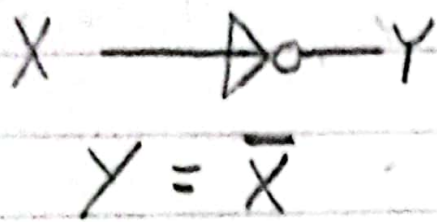
- 1) Boolean logic : It is important for computer science because ~~#~~ it fits with binary number system in which each bit has the value of 0 ~~or~~ or 1.
- 2) Logic gates : It is an electronic circuit which operates on one or more input signals to produce an output signal.
- 3) Truth table : It is a tabular representation of all the combinations of values for inputs and their corresponding output.
- 4) NOT Gate (Inverter gate) : It is a gate with only one input and only one output signal. The output is always opposite of input.



Truth table

X	$Y = \bar{X}$
0	1
1	0

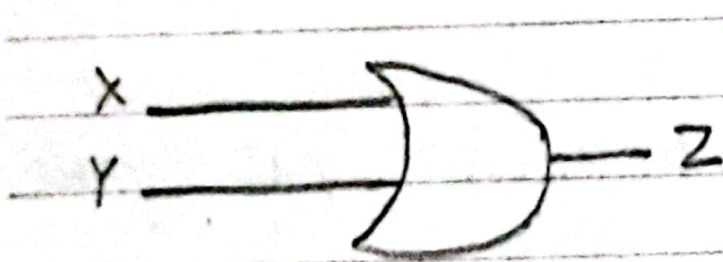
5) OR gate : It has two or more input signals but only one output signal. If any one of the input signal is 1, Then the output signal is always 1.



$$Z = X + Y$$

Input		Output
X	Y	$Z = X + Y$
0	0	0
0	1	1
1	0	1
1	1	1

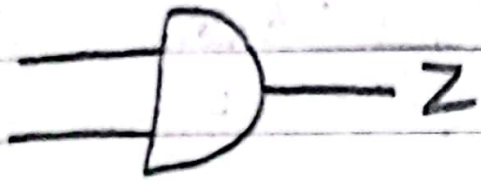6) AND gate : It has two or more input signals but only one output signal. If all the input signals are 1, Then the output signal will be 1. Otherwise it will be 0.




$$Z = X \cdot Y$$

X	Y	Z = X · Y
0	0	0
0	1	0
1	0	0
1	1	1

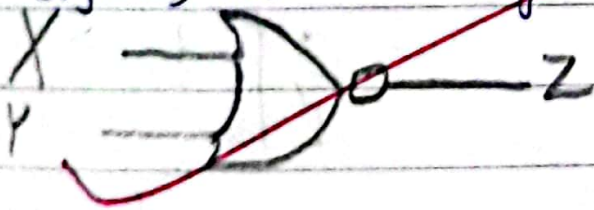7) NOR gate (NOT + OR)


It has two or more input signals but only one output signal. If all the inputs ~~is~~ are low then the output signals will be high.



Truth Table


Input		Output
X	Y	X + Y
0	0	1
0	1	0
1	0	0
1	1	0

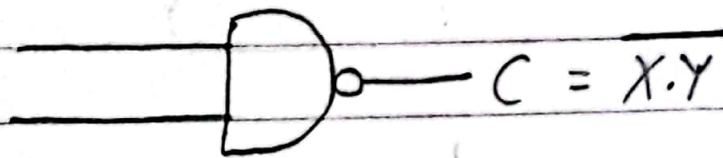8) NAND gate (NOT + AND): It has two or more input signals but only one output signal. If all the inputs are high, then the output will be low.



X	Y	X NAND Y
0	0	1
0	1	1
1	0	1
1	1	0

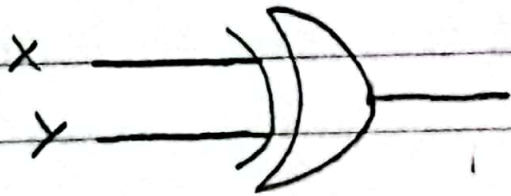9) XOR Gate : XOR gate produces output 1 for only those input combinations that have odd number of ones.



X	Y	X XOR Y
0	0	0
0	1	1
1	0	1
1	1	0

10) De Morgan's Law : De Morgan's states that

i) $\overline{XY} = \overline{X} + \overline{Y}$

ii) $\overline{X+Y} = \overline{X} \cdot \overline{Y}$

Proving $\overline{XY} = \overline{X} + \overline{Y}$

X	Y	$X \cdot Y$	$\overline{X \cdot Y}$	$\overline{X}$	$\overline{Y}$	$\overline{X + Y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

LHS RHS

$$LHS = RHS$$

Proving $X + Y = \overline{X \cdot Y}$

X	Y	$X + Y$	$\overline{X}$	$\overline{Y}$	$\overline{X \cdot Y}$
0	0	0	1	1	1
0	1	1	1	0	0
1	0	1	0	1	0
1	1	1	0	0	0

LHS RHS

$$LHS = RHS$$

Prove the following boolean expressions using truth table

i) $X + \overline{X}Y = X + Y$

X	Y	$\bar{X}$	$\bar{X} \cdot Y$	$X + \bar{X}Y$	$X + Y$
0	0	1	0	0	0
0	1	1	1	1	1
1	0	0	0	1	1
1	1	0	0	1	1

LHS

RHS

$$RHS = LHS$$

$$ii) A + \bar{A}\bar{B} = A + \bar{B}$$

A	B	$\bar{A}$	$\bar{B}$	$\bar{A}\bar{B}$	$A + \bar{A}\bar{B}$	$A + \bar{B}$
0	0	1	1	1	1	1
0	1	1	0	0	0	0
1	0	0	1	0	1	1
1	1	0	0	0	1	1

LHS

RHS

$$iii) (X+Y)(X+Z) = X + YZ$$

X	Y	Z	$X+Y$	$X+Z$	$(X+Y)(X+Z)$	YZ	$X+YZ$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1


LHS RHS

$$LHS = RHS$$


11) Logic Circuits : It's a diagram used to represent boolean logic gates. The diagram is known as Logic Circuits.

12) Draw the logic circuit of following questions.


i) $X + \bar{X}Y$

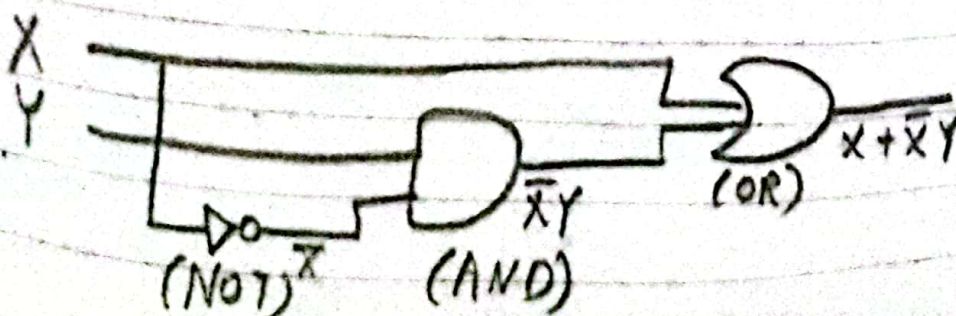


ii) $\bar{A}\bar{B} + AC$

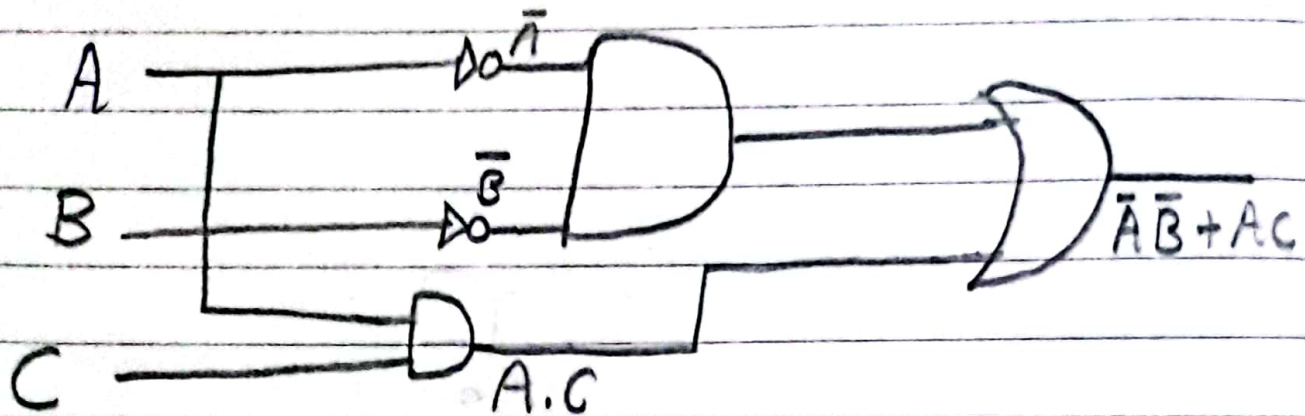


iii) $(U+V) \cdot (V'+W')$

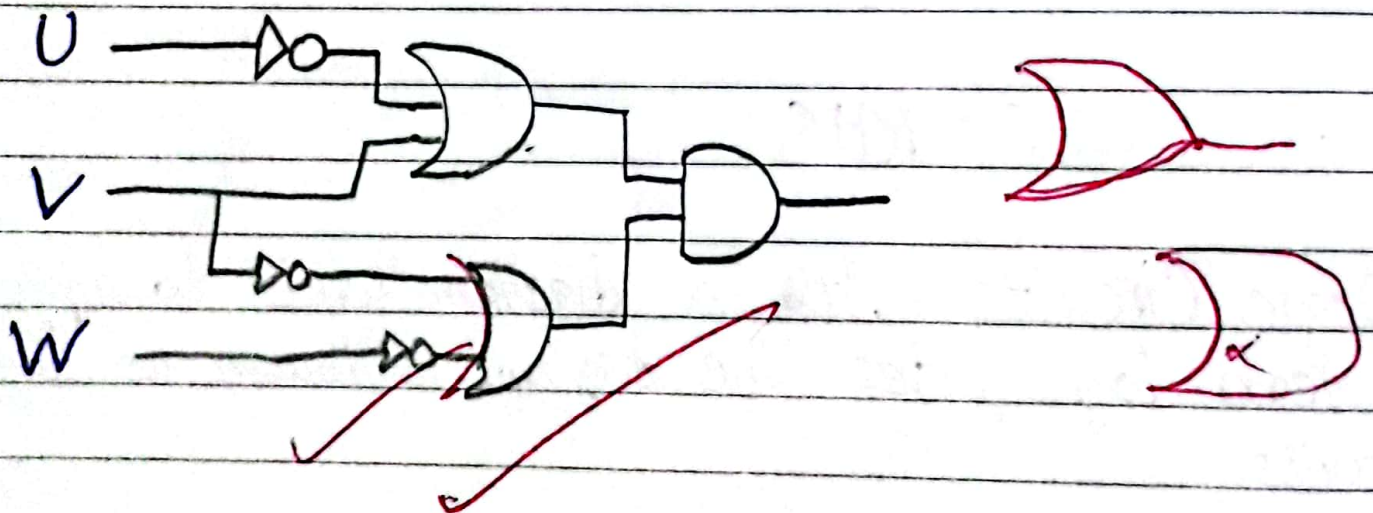

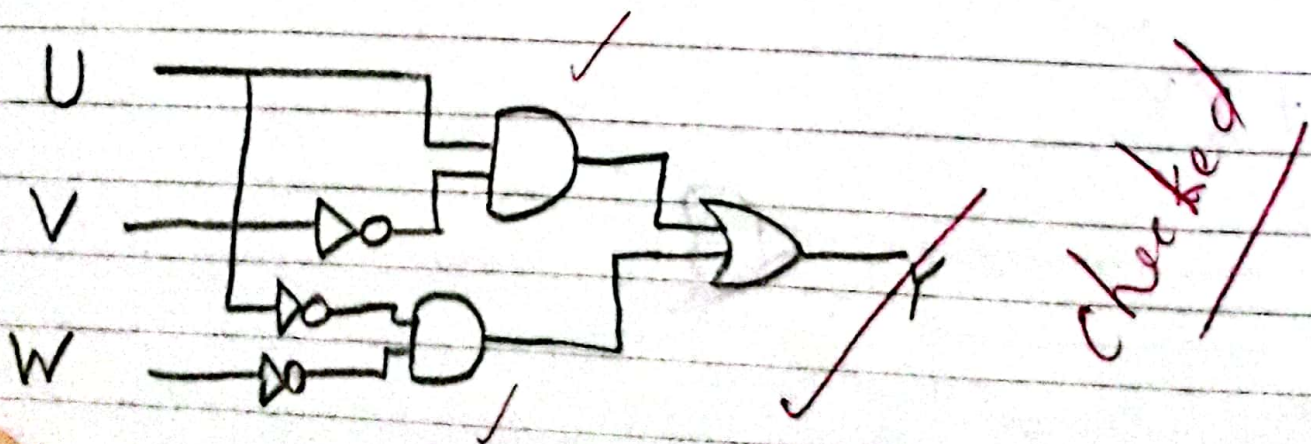
iv) $Y = (U \cdot \bar{V}) + (\bar{U} \cdot W)$




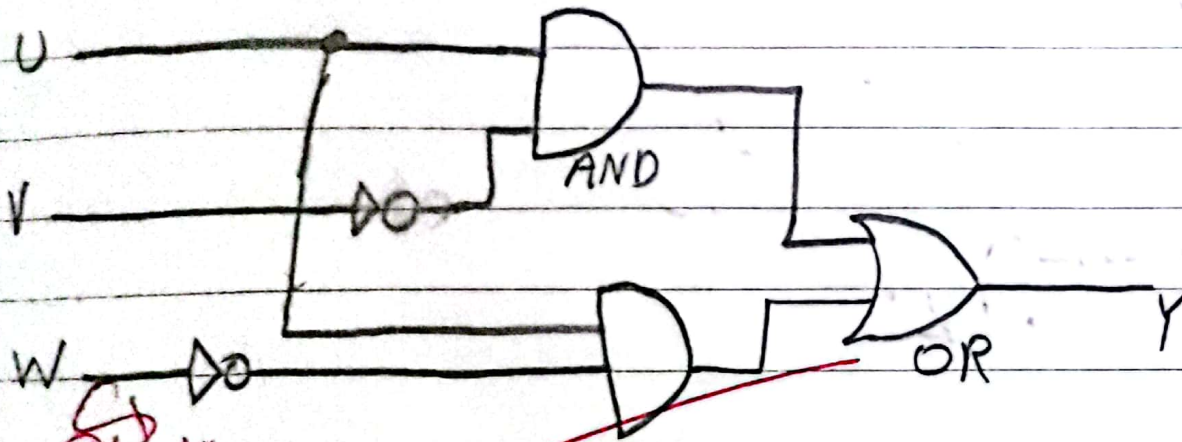
$$v) Y = (U \cdot V) + (\bar{U} \cdot \bar{W})$$



$$vi) A'B + A'C$$

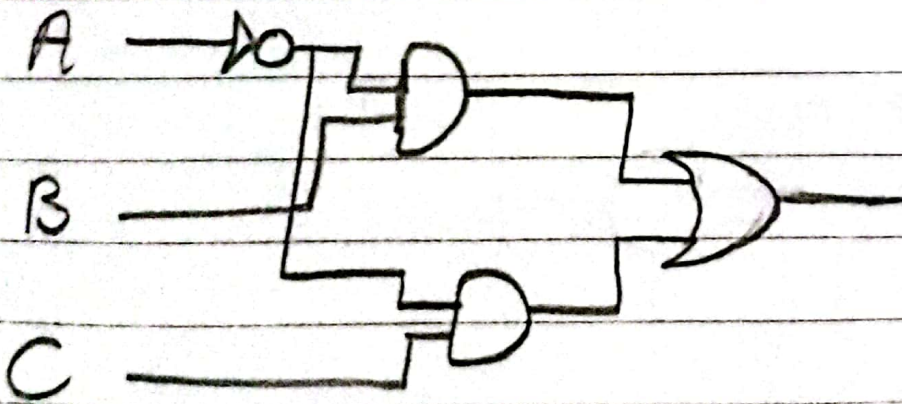

vii) $AB + \bar{A}C$

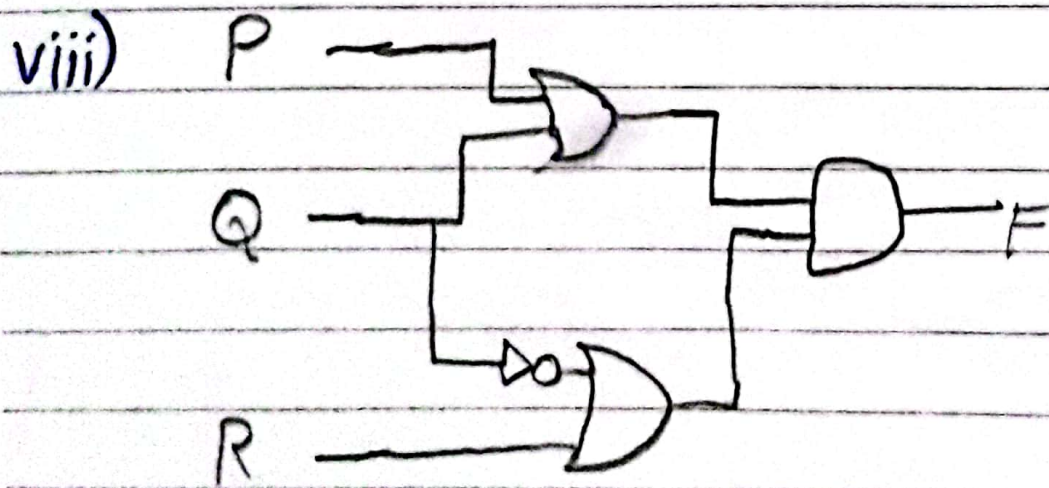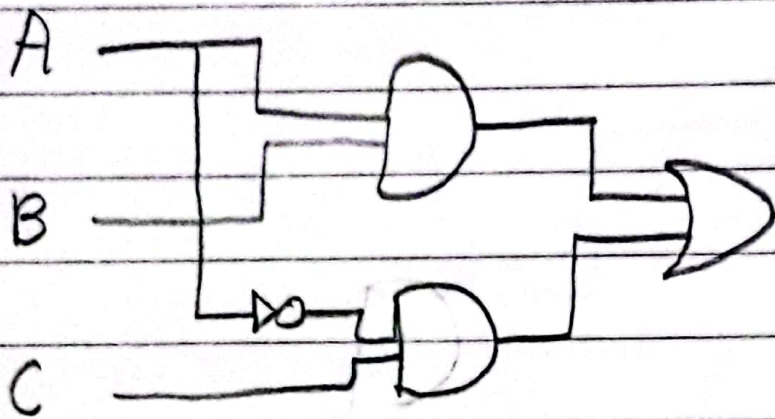

$$\bar{A}R \quad (P + Q) \cdot (\bar{Q} + R) = F$$